

CS 312: Computer Architecture II

Name: Orchlon Chinbat

Student ID: 50291063

Honor Code: I pledge that this submission is all my own work and not a copy nor a partial copy from anywhere.

Lab 1. The AND, OR, NAND and NOR logic gates.


Use the MultimediaLogic (MMLLogic) system to set up the following circuit: $F = AB + CD$

Use four switches for controlling the inputs and an LED to show the value of F.

Part 1. a). Simulate the circuit for all combinations of A, B, C, and D and record the results. Use a truth table to show these results.

A	B	C	D	AB	CD	$F = AB + CD$
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	1	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	0	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	0	1	1
1	1	0	0	1	0	1
1	1	0	1	1	0	1
1	1	1	0	1	0	1
1	1	1	1	1	1	1


Part 1. b) Sketch or copy/paste screenshot of your circuit that you make in MM logic circuit here.

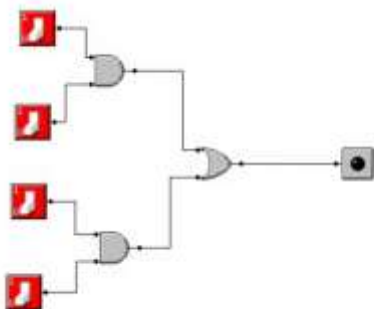

Part 2. a) Change the OR gate to a NOR gate. Simulate the circuit and record the results in a truth table.

A	B	C	D	AB	CD	F = AB NOR CD
0	0	0	0	0	0	1
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	0	0	1
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	1	0

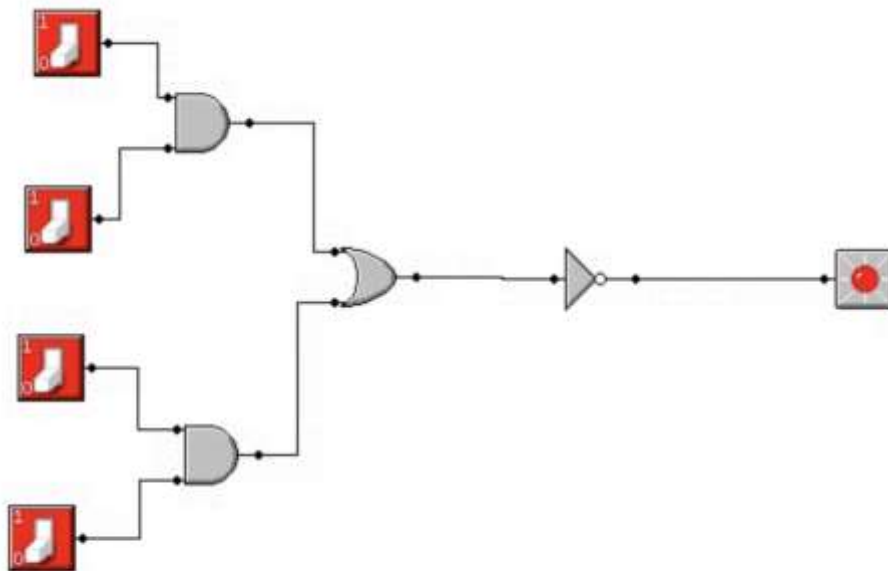Part 2. b) Draw the circuit (in all tasks copy a screenshot of your circuit that you make in MM logic). For the part2, the OR gate is changed to a new NOR gate.



Part 2. c) Write the equation for this new circuit, forming the equation based on the circuit diagram and not on the Truth Table. Apply **DeMorgan's Theorem** to this equation and apply again until you get a product of sums. Expand the product of sums to get the sum of products equation.

1. Original NOR circuit: $F = (AB+CD)'$
2. Now, apply DeMorgan's Theorem again to each negated product, since $(X \cdot Y)' = X' + Y'$:
 - $F = (AB)' \cdot (CD)' = (A' + B') \cdot (C' + D')$
3. Expand to Sum of Products:
 - $F = (A' + B') \cdot (C' + D') = A'C' + A'D' + B'C' + B'D'$

(SOP) form is: $F = A'C' + A'D' + B'C' + B'D'$

Part 3.a) Product of sums:

Base on the truth table from 2a, applying that the output is 1 if none of the input combinations that produce 0 is true, write out the equation. Apply the DeMorgan's Theorem to it and convert it into the POS form:

Answer:

$$F = (A+B+C'+D')(A+B'+C'+D')(A'+B+C'+D')(A'+B'+C+D)(A'+B'+C+D')(A'+B'+C'+D)(A'+B'+C'+D')$$

Part 3.b) Sum of products:

Base on the truth table from 2a, applying that the output F is 1 if any of the input combinations that produces 1 is true, write the equation in an SOP form:

Answer:

$$F = A'B'C'D' + A'B'C'D + A'B'CD' + A'BC'D' + A'BC'D + A'BCD' + AB'C'D' + AB'C'D + AB'CD'$$

Show that the SOP form is equivalent to the equation in 2c:

Answer:

$$F = A'C' + A'D' + B'C' + B'D' = (A' + B')(C' + D')$$

Grading rubric:

Parts	Points
Part 1.a	5
Part 1.b	5
Part 2.a	5
Part 2.b	5
Part 2.c	5
Part 3.a	5

Part 3.b	5
----------	---

Submission:

This file must be submitted through Canvas.